
PROJECT STEP 3

TURING MACHINE

List of Group Members

Brandon Markham

Paul Henson

Sam Arshad

CS.3339 Computer Architecture

Texas State University

April 16, 2024

1 Introduction

For this final step of the project, the Turing Machine group implemented, tested and integrated our Verilog code into one package. We used an online web editor and compiler called "EDA Playground". We implemented behavioral-level logic to accomplish these tasks, and used EDA Playground's waveform generator feature in order to visualize the waveform(s).

2 Verilog Modules

In this section, we were required to assemble each previously-created bitwise logic and arithmetic functions into a top-level ALU module. Each module presented below (outside of the final ALU module) are written and function the same as they did in the previous reports with one exception in the bitshifting operation, which is described in its subsection.

2.1 MultiBit AND

```
1 module multibit_AND
2   #(parameter WIDTH = 4) (
3     input [WIDTH-1 : 0] a, input [WIDTH-1 : 0] b,
4     output [WIDTH-1 : 0] out);
5   assign out = a & b;
6 endmodule
```

2.2 MultiBit NAND

```
1 module multibit_NAND
2   #(parameter WIDTH = 4) (
3     input [WIDTH-1 : 0] a, input [WIDTH-1 : 0] b,
4     output [WIDTH-1 : 0] out);
5   assign out = ~(a & b);
6 endmodule
```

2.3 MultiBit OR

```
1 module multibit_OR
2   #(parameter WIDTH = 4) (
3     input [WIDTH-1 : 0] a, input [WIDTH-1 : 0] b,
4     output [WIDTH-1 : 0] out);
5   assign out = a | b;
```

```
6 endmodule
```

2.4 MultiBit NOR

```
1 module multibit_NOR
2   #(parameter WIDTH = 4) (
3     input [WIDTH-1 : 0] a, input [WIDTH-1 : 0] b,
4     output [WIDTH-1 : 0] out);
5   assign out = ~(a | b);
6 endmodule
```

2.5 MultiBit XOR

```
1 module multibit_XOR
2   #(parameter WIDTH = 4) (
3     input [WIDTH-1 : 0] a, input [WIDTH-1 : 0] b,
4     output [WIDTH-1 : 0] out);
5   assign out = a ^ b;
6 endmodule
```

2.6 MultiBit XNOR

```
1 module multibit_XNOR
2   #(parameter WIDTH = 4) (
3     input [WIDTH-1 : 0] a, input [WIDTH-1 : 0] b,
4     output [WIDTH-1 : 0] out);
5   assign out = a ^^ b;
6 endmodule
```

2.7 MultiBit NOT

```
1 module multibit_NOT
2   #(parameter WIDTH = 4) (
3     input [WIDTH-1 : 0] a,
4     output [WIDTH-1 : 0] out);
5   assign out = ~a;
6 endmodule
```

2.8 Binary Adder

```
1 module binaryAdder
2   #(parameter WIDTH = 4) (
3     input [WIDTH-1 : 0] a,
4     input [WIDTH-1 : 0] b,
5     input carryin,
```

```

6     output [WIDTH-1 : 0] out,
7     output carryout );
8
9     reg [WIDTH : 0] ans;
10
11    always @(*) begin
12
13        ans = a + b + carryin;
14
15    end
16
17    assign out = ans[WIDTH-1 : 0];
18    assign carryout = ans[WIDTH];
19
20 endmodule

```

2.9 Binary Subtractor

```

1 module binarySubtractor
2     #(parameter WIDTH = 4) (
3         input [WIDTH-1 : 0] a,
4         input [WIDTH-1 : 0] b,
5         input carryin,
6         output [WIDTH-1 : 0] out,
7         output carryout );
8
9     reg [WIDTH : 0] ans;
10
11    always @(*) begin
12
13        ans = {1'b1,a};
14        ans = ans - b - carryin;
15
16
17    end
18
19    assign carryout = ~ans[WIDTH];
20    assign out = ans[WIDTH-1 : 0];
21
22 endmodule

```

2.10 Binary Multiplier

```

1 module binaryMultiplier

```

```

2  #(parameter WIDTH = 4) (
3      input  [WIDTH-1 : 0] a,
4      input  [WIDTH-1 : 0] b,
5      output [WIDTH-1 : 0] MSB,
6      output [WIDTH-1 : 0] LSB );
7
8      reg [(2*WIDTH)-1 : 0] ans;
9
10     always @(*) begin
11
12         ans = a * b;
13
14     end
15
16     assign LSB = ans[WIDTH-1 : 0];
17     assign MSB = ans[(2*WIDTH)-1 : WIDTH];
18
19 endmodule

```

2.11 Binary Dividor

```

1 module binaryDivider
2     #(parameter WIDTH = 4) (
3         input  [WIDTH-1 : 0] a,
4         input  [WIDTH-1 : 0] b,
5         output reg [WIDTH-1 : 0] ans,
6         output reg [WIDTH-1 : 0] rem );
7
8     always @(*) begin
9
10        ans = a / b;
11        rem = a % b;
12
13    end
14
15 endmodule

```

2.12 Multi Bit Shifter

Notable Version Change: Lines 22 and 36. The continuation criteria of two for loops were expanded from the previous version in order to create an upper ceiling on the number of loops that were possible to be requested by the control input.

```

1 module multiShift

```

```

2  #(parameter WIDTH = 4) (
3      input [WIDTH-1 : 0] in,
4      input [WIDTH-1 : 0] control,
5      output reg [WIDTH-1 : 0] outSubject,
6      output reg [WIDTH-1 : 0] outOverflow );
7
8  reg [(2*WIDTH)-1 : 0] ans;
9
10 wire dir  = control[WIDTH-1]; // 1 <-- left ; right --> 0
11 wire fill = control[0];
12 wire [WIDTH-1 - 2 : 0] amt = control[WIDTH-1 - 1 : 1];
13
14 integer i;
15
16 always @(*) begin
17     //$display("in = %b, control = %b, dir = %b, fill = %b, amt = %b", in,
18     control, dir, fill, amt);
19     if (dir) begin
20         ans = in << amt;
21         //$display("ans shifted = %b", ans);
22         if(amt>0) begin
23             for (i = 0; (i < amt) && (i < WIDTH*2); i = i+1) begin
24                 ans[i] = fill;
25             end
26             //$display("ans filled  = %b", ans);
27             outSubject  = ans[WIDTH-1 : 0];
28             outOverflow = ans[(2*WIDTH)-1 : WIDTH];
29         end
30     else begin
31         ans = in << WIDTH;
32         //$display("ans before  = %b", ans);
33         ans = ans >> amt;
34         //$display("ans shifted = %b", ans);
35         if(amt>0) begin
36             for(i = 0; (i < amt) && (i < WIDTH*2); i = i+1) begin
37                 ans[(2*WIDTH-1) - i] = fill;
38             end
39             //$display("ans filled  = %b", ans);
40             outSubject  = ans[(2*WIDTH)-1 : WIDTH];
41             outOverflow = ans[WIDTH-1 : 0];
42         end
43     end

```

```

44
45     end
46
47
48 endmodule

```

3 ALU

The ALU module instantiates each of the modules shown above, and handles routing outputs from the operation selected via an input operation code (opcode).

```

1 module ALU
2     #(parameter WIDTH = 4) (
3         input  [3:0] opcode,
4         input  [WIDTH-1 : 0] a,
5         input  [WIDTH-1 : 0] b,
6         input  carryin,
7         output reg [WIDTH-1 : 0] out,
8         output reg [WIDTH-1 : 0] extra );
9
10    wire [WIDTH-1 : 0] and_out;
11    wire [WIDTH-1 : 0] nand_out;
12    wire [WIDTH-1 : 0] or_out;
13    wire [WIDTH-1 : 0] nor_out;
14    wire [WIDTH-1 : 0] xnor_out;
15    wire [WIDTH-1 : 0] xor_out;
16    wire [WIDTH-1 : 0] not_out;
17
18    multibit_AND #(.WIDTH( WIDTH )) alu_AND (
19        .a( a ),
20        .b( b ),
21        .out( and_out ));
22    multibit_NAND #(.WIDTH( WIDTH )) alu_NAND (
23        .a( a ),
24        .b( b ),
25        .out( nand_out ));
26    multibit_OR #(.WIDTH( WIDTH )) alu_OR (
27        .a( a ),
28        .b( b ),
29        .out( or_out ));
30    multibit_NOR #(.WIDTH( WIDTH )) alu_NOR (
31        .a( a ),
32        .b( b ),

```

```

33     .out( nor_out ));
34 multibit_XOR #(.WIDTH( WIDTH )) alu_XOR (
35     .a( a ),
36     .b( b ),
37     .out( xor_out ));
38 multibit_XNOR #(.WIDTH( WIDTH )) alu_XNOR (
39     .a( a ),
40     .b( b ),
41     .out( xnor_out ));
42 multibit_NOT #(.WIDTH( WIDTH )) alu_NOT (
43     .a( a ),
44     .out( not_out ));
45
46
47 wire [WIDTH-1 : 0] add_out;
48 wire [WIDTH-1 : 0] add_carryout;
49 wire [WIDTH-1 : 0] sub_out;
50 wire [WIDTH-1 : 0] sub_carryout;
51 wire [WIDTH-1 : 0] mul_msb;
52 wire [WIDTH-1 : 0] mul_lsb;
53 wire [WIDTH-1 : 0] div_ans;
54 wire [WIDTH-1 : 0] div_rem;
55
56 binaryAdder #(.WIDTH( WIDTH )) alu_add (
57     .a( a ),
58     .b( b ),
59     .carryin( carryin ),
60     .out( add_out ),
61     .carryout( add_carryout ));
62 binarySubtractor #(.WIDTH( WIDTH )) alu_sub (
63     .a( a ),
64     .b( b ),
65     .carryin( carryin ),
66     .out( sub_out ),
67     .carryout( sub_carryout ));
68 binaryMultiplier #(.WIDTH( WIDTH )) alu_mul (
69     .a( a ),
70     .b( b ),
71     .MSB( mul_msb ),
72     .LSB( mul_lsb ));
73 binaryDivider #(.WIDTH( WIDTH )) alu_div (
74     .a( a ),
75     .b( b ),

```



```
76     .ans( div_ans ),
77     .rem( div_rem ));
78
79 wire [WIDTH-1 : 0] shf_sub;
80 wire [WIDTH-1 : 0] shf_ovr;
81 multiShift #(WIDTH( WIDTH )) alu_shf (
82     .in( a ),
83     .control( b ),
84     .outSubject( shf_sub ),
85     .outOverflow( shf_ovr ));
86
87
88 always_comb begin
89
90     case(opcode)
91         4'b0000 : out = and_out;
92         4'b0001 : out = or_out;
93         4'b0010 : out = nand_out;
94         4'b0011 : out = nor_out;
95         4'b0100 : out = xor_out;
96         4'b0101 : out = xnor_out;
97         4'b0110 : out = not_out;
98         4'b0111 : begin
99             out = add_out;
100             extra = add_carryout;
101         end
102         4'b1000 : begin
103             out = sub_out;
104             extra = sub_carryout;
105         end
106         4'b1001 : begin
107             out = mul_msb;
108             extra = mul_lsb;
109         end
110         4'b1010 : begin
111             out = div_ans;
112             extra = div_rem;
113         end
114         4'b1011 : begin
115             out = shf_sub;
116             extra = shf_ovr;
117         end
118     endcase
```

```
119
120     end
121
122
123
124
125 endmodule
```

4 Verilog Testbench

The testbench was designed in such a way as to be able to test ALU modules with widths of multiples of 4, defined by a WIDTH parameter on line 2 of the testbench file. The tested variables used Verilog's replication operator in order to generate useful input commands of varying length.

In testing, the WIDTH parameter was scaled to values 4, 8, 16, and 32 in order to test higher ALU register sizes.

```
1 module testbench
2     #(parameter WIDTH = 32);
3
4     reg [3:0] opcode;
5     reg [WIDTH-1 : 0] a;
6     reg [WIDTH-1 : 0] b;
7     reg carryin;
8
9     reg [WIDTH-1 : 0] out;
10    reg [WIDTH-1 : 0] extra;
11
12    ALU #(.WIDTH( WIDTH )) alu (
13        .opcode( opcode ),
14        .a( a ),
15        .b( b ),
16        .carryin( carryin ),
17        .out( out ),
18        .extra( extra ));
19
20    integer i;
21
22    initial begin
23
24        // Dump waves to file to be read by wave viewer
25        $dumpfile("dump.vcd");
```

```
26    $dumpvars(1);
27
28
29    for(i = 0; i < 12; i += 1) begin
30        opcode = i;
31        a = {WIDTH/4{4'b1010}};
32        b = {WIDTH/4{4'b0101}};
33        carryin = 0;
34        #1;
35        a = {WIDTH/4{4'b0110}};
36        b = {WIDTH/4{4'b0110}};
37        carryin = 1;
38        #1;
39
40    end
41
42
43 end
44
45 endmodule
```

5 Waveform Test

Shown below are the output waveform tables generated by testing.

Opcode interpretations and "extra" output signal labels have been added to each waveform table image for ease of interpretation.

5.0.1 GATES

 


Figure 1: 4-bit wide bitwise logic functions.

5.0.2 OPERATIONS

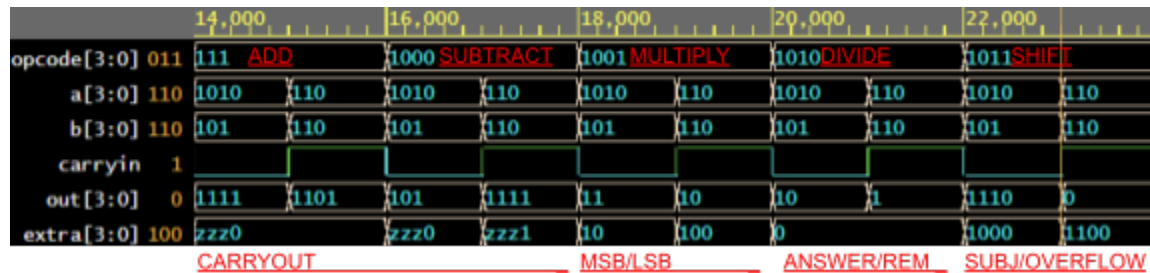


Figure 2: 4-bit wide arithmetic operations.

5.1 Extra Credit: Higher-Width Register Waveforms

5.1.1 8, 16, 32 bit Gates and Operations

Higher-width register testing waveforms shown below have signal values listed in hexadecimal to accommodate reasonable viewing.

 


Figure 3: 8-bit wide bitwise logic functions.

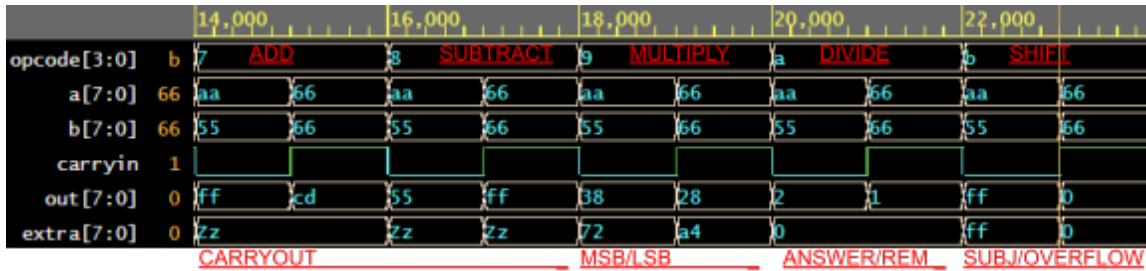


Figure 4: 8-bit wide arithmetic operations.

 


Figure 5: 16-bit wide bitwise logic functions.

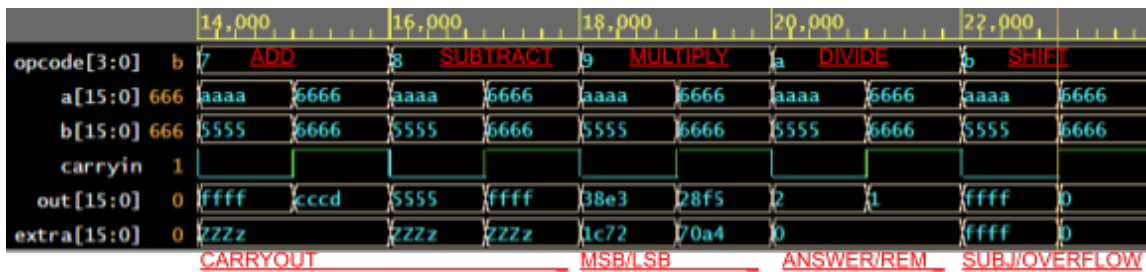


Figure 6: 16-bit wide arithmetic operations.

	0	2,000	4,000	6,000
opcode[3:0]	5 0 AND	1 OR	2 NAND	3 NOR
a[31:0]	aaa aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666
b[31:0]	555 5555_5555 6666_6666	5555_5555 6666_6666	5555_5555 6666_6666	5555_5555 6666_6666
carryin	0			
out[31:0]	0 0	6666_6666 ffff_ffff	6666_6666 ffff_ffff	9999_9999 0 9999_9999
extra[31:0]	xxx xxxx_xxxx			

Figure 7: 32-bit wide bitwise logic functions, table 1 of 2.

	8,000	10,000	12,000
opcode[3:0]	5 4 XQR	5 XNOR	6 NOT
a[31:0]	aaa aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666
b[31:0]	555 5555_5555 6666_6666	5555_5555 6666_6666	5555_5555 6666_6666
carryin	0		
out[31:0]	0 ffff_ffff 0	ffff_ffff 5555_5555	9999_9999
extra[31:0]	xxx		

Figure 8: 32-bit wide bitwise logic functions, table 2 of 2.

	14,000	15,000	16,000	17,000
opcode[3:0]	5 7		8	
a[31:0]	aaa aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666
b[31:0]	555 5555_5555 6666_6666	5555_5555 6666_6666	5555_5555 6666_6666	5555_5555 6666_6666
carryin	0			
out[31:0]	0 ffff_ffff	cccc_cccd	5555_5555	ffff_ffff
extra[31:0]	xxx 2222_2222		2222_2222	2222_2222

CARRYOUT

Figure 9: 32-bit wide arithmetic operations, table 1 of 2. Add and Subtract operations shown in order.

	18,000	19,000	20,000	21,000	22,000	23,000
opcode[3:0]	5 9		a		b	
a[31:0]	aaa aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666	aaaa_aaaa 6666_6666
b[31:0]	555 5555_5555 6666_6666	5555_5555 6666_6666	5555_5555 6666_6666	5555_5555 6666_6666	5555_5555 6666_6666	5555_5555 6666_6666
carryin	0					
out[31:0]	0 88e1_8e38	28f5_c28f	2	1	ffff_ffff	0
extra[31:0]	xxx 71c7_1c72	a3d_70a4	0		ffff_ffff	0

MSB/LSB ANSWER/REM SUB./OVERFLOW

Figure 10: 32-bit wide arithmetic operations, table 2 of 2. Multiply, Divide, and Bitshift operations shown in order.

6 Conclusion

This final segment of the project required very little extra overhead in terms of learning and work as compared to the previous two parts. The testbench was, by now, a familiar format that required only one novel technique in the form of parametrizable variable generation via the replication operator.

Notably, Verilog's switch (case) statement was implemented for the first time in this project inside of the ALU module. Otherwise, only one small adjustment was required between the previously created modules.

The majority of the group's effort for this section was in compiling and verifying the outputs of each test case rather than in learning and writing code, which is nonetheless likely representative of many real-world tasks we may encounter in the future.

As closing notes for the entirety of this project, the members of our group have gained a valuable understanding of both a hardware descriptive language and an advanced markup document-creation language, have gained a sense for the amount of work that must be put in to learn new languages without actively guidance, and have learned a lesson about fully exploring the confines of an assignment and requesting clarification before misguidedly reinventing the wheel.